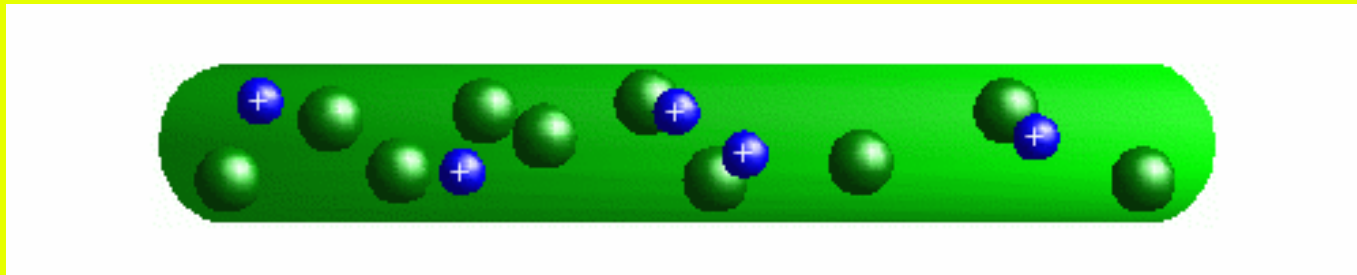




Electricity

- **Voltage (V)** depends on the distance between charges.
- **Current (C)** depends on the number of moving charges.
- **Resistance (R)** depends on how much moving charges are slowed down




Electricity

 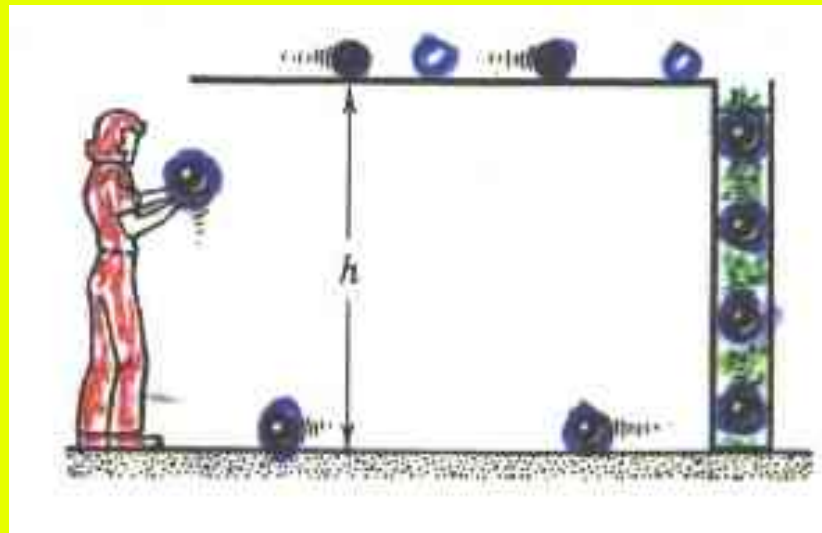- **Voltage (V)** depends on the distance between charges.




Electricity

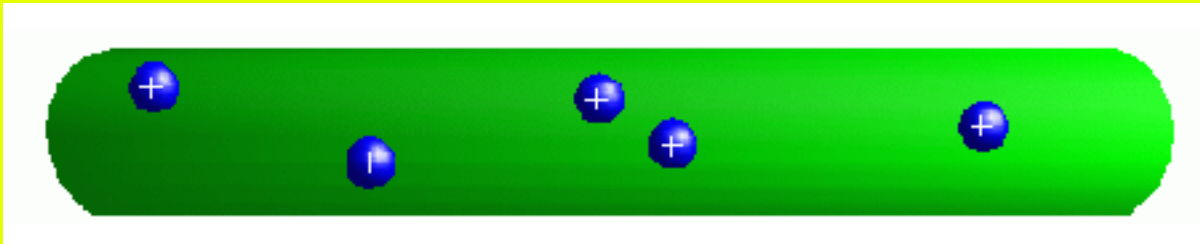- **Voltage** (**V**) depends on the distance between charges.
- **Current** (**C**) depends on the number of moving charges.




Small Current

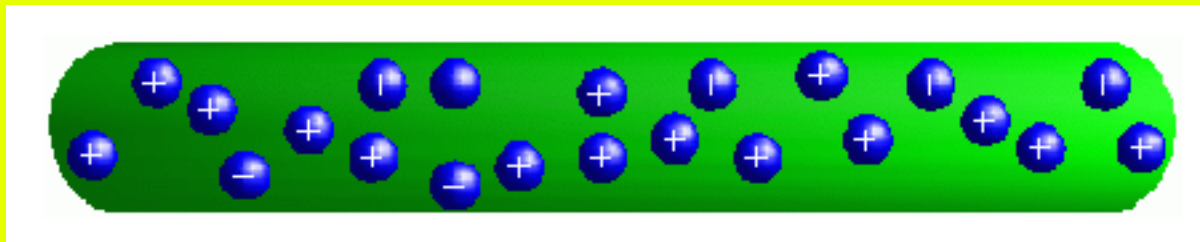

Large Current

Electricity

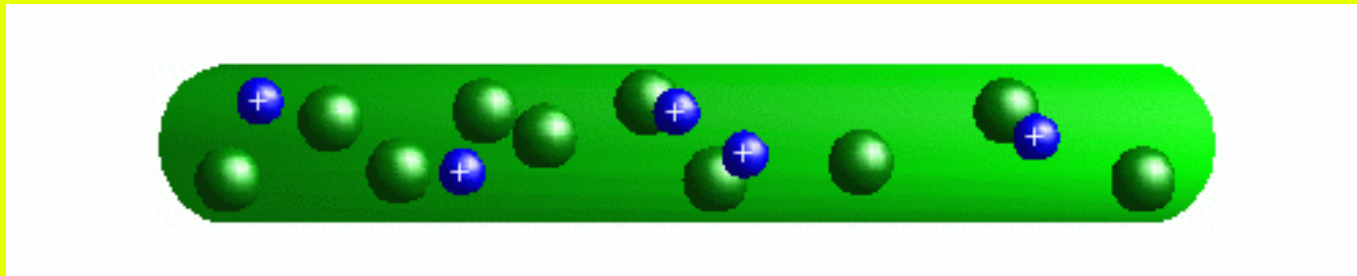- **Voltage (V)** depends on the distance between charges.
- **Current (C)** depends on the number of moving charges.
- **Resistance (R)** depends on how much moving charges are slowed down



Electricity

- **Voltage (V)** depends on the distance between charges.
- **Current (C)** depends on the number of moving charges.
- **Resistance (R)** depends on how much moving charges are slowed down.
- A formula which describes how **voltage**, **current** and **resistance** depend on each other is:

$$\mathbf{V} = \mathbf{C} \times \mathbf{R} \quad \text{or} \quad \mathbf{C} = \mathbf{V} / \mathbf{R}$$

Electricity

- **Voltage (V)** depends on the distance between charges.
- **Current (C)** depends on the number of moving charges.
- **Resistance (R)** depends on how much moving charges are slowed down.
- A formula which describes how **voltage**, **current** and **resistance** depend on each other is:

$$\mathbf{V} = \mathbf{C} \times \mathbf{R} \quad \text{or} \quad \mathbf{C} = \mathbf{V} / \mathbf{R}$$

- Example:
 - If the **current** is $\mathbf{C} = 2$ and the **resistance** is $\mathbf{R} = 100$, how large is the **voltage (V)**?

Electricity



- **Voltage (V)** depends on the distance between charges.
- **Current (C)** depends on the number of moving charges.
- **Resistance (R)** depends on how much moving charges are slowed down.
- A formula which describes how **voltage**, **current** and **resistance** depend on each other is:

$$\mathbf{V} = \mathbf{C} \times \mathbf{R} \quad \text{or} \quad \mathbf{C} = \mathbf{V} / \mathbf{R}$$

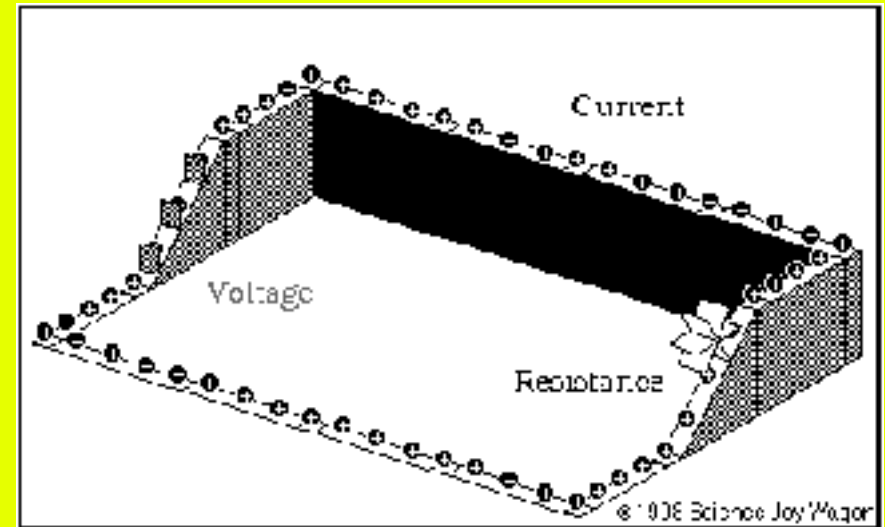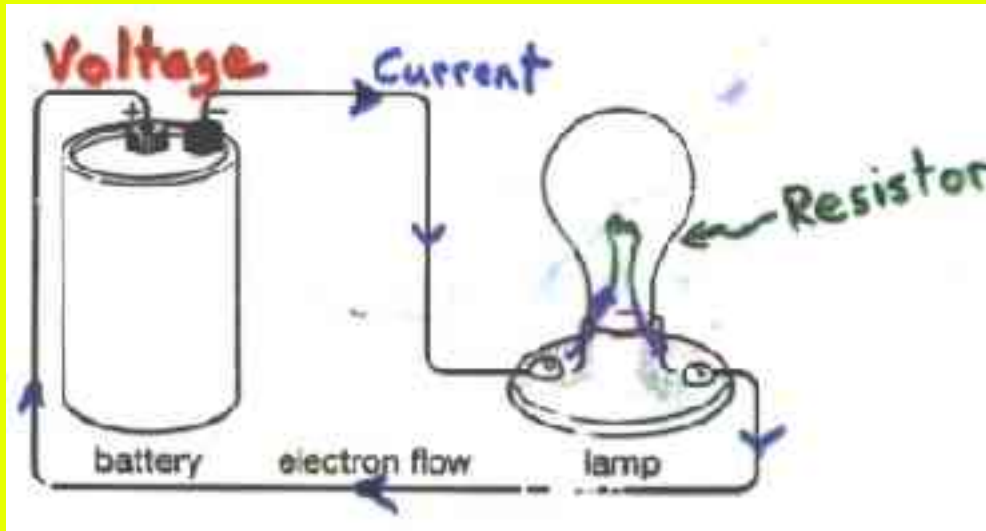- Example:
 - If the **current** is $\mathbf{C} = 2$ and the **resistance** is $\mathbf{R} = 100$, how large is the **voltage (V)**?

Electricity

- Simple circuit to show how current depends on voltage




Resistance -- tries to stop current!

Current -- charges flowing through wire

Voltage – separates charges

Electricity

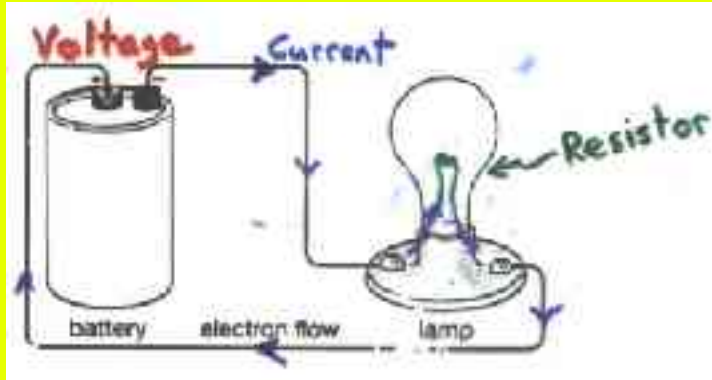- Simple circuit to show how current depends on voltage:




Table

Voltage **Current**

Electricity

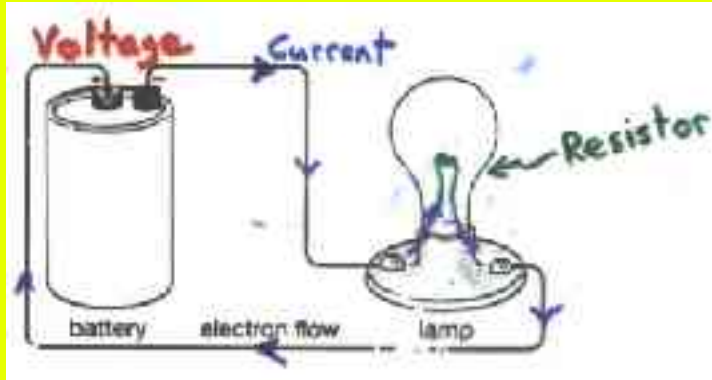- Simple circuit to show how current depends on voltage:




Table

Voltage	Current
---------	---------

0.	0.
----	----

Electricity

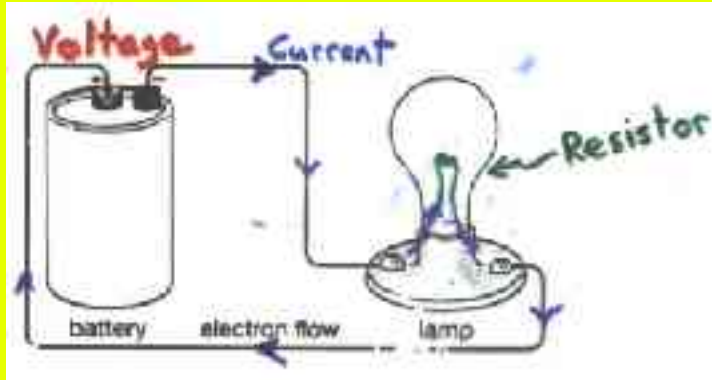- Simple circuit to show how current depends on voltage:




Table

Voltage	Current
---------	---------

0.	0.
----	----

Electricity

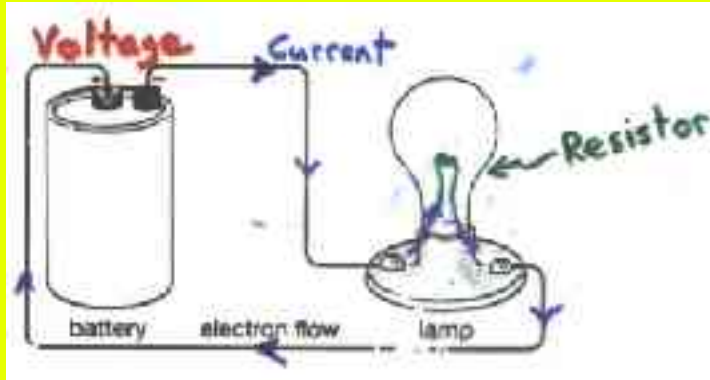- Simple circuit to show how current depends on voltage:



Table


Voltage	Current
---------	---------

0.	0.
----	----

40.	185.
-----	------

Electricity

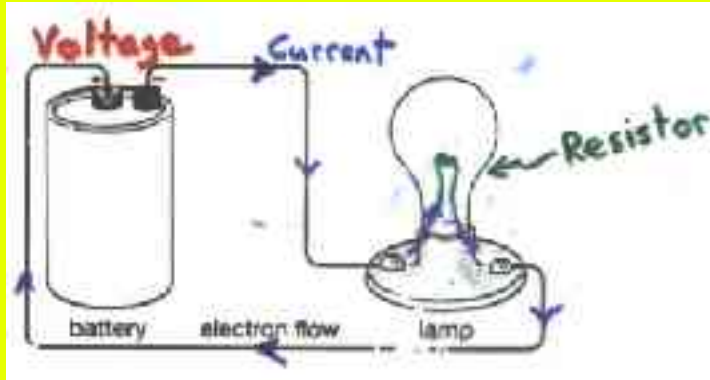- Simple circuit to show how current depends on voltage:



Table

Voltage **Current**


0. 0.

40. 185.

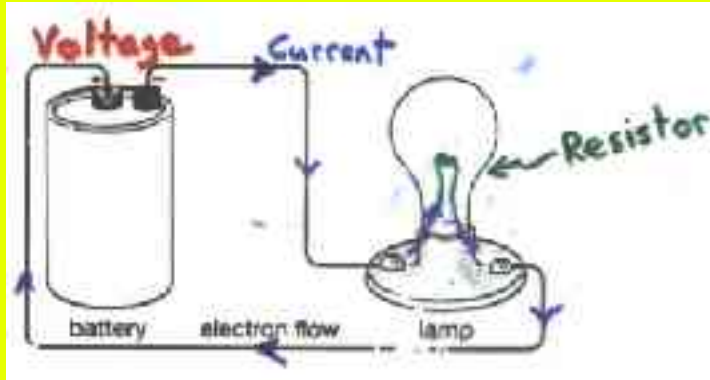80. 260.

Electricity

- Simple circuit to show how current depends on voltage:



Table

Voltage **Current**

0. 0.


40. 185.

80. 260.

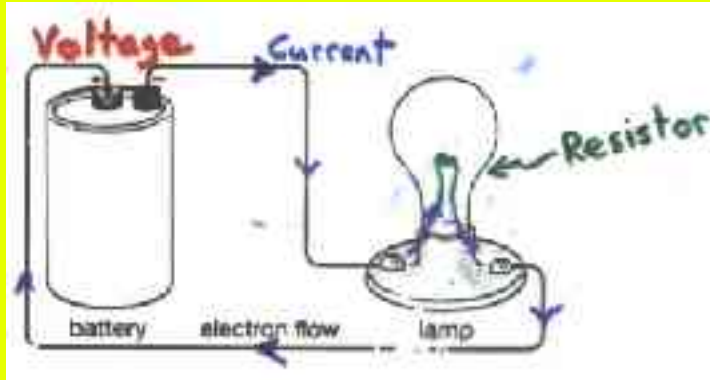120. 317.

Electricity


- Simple circuit to show how current depends on voltage:



Table


Voltage **Current**

0.	0.
40.	182.
80.	254.
120.	315.

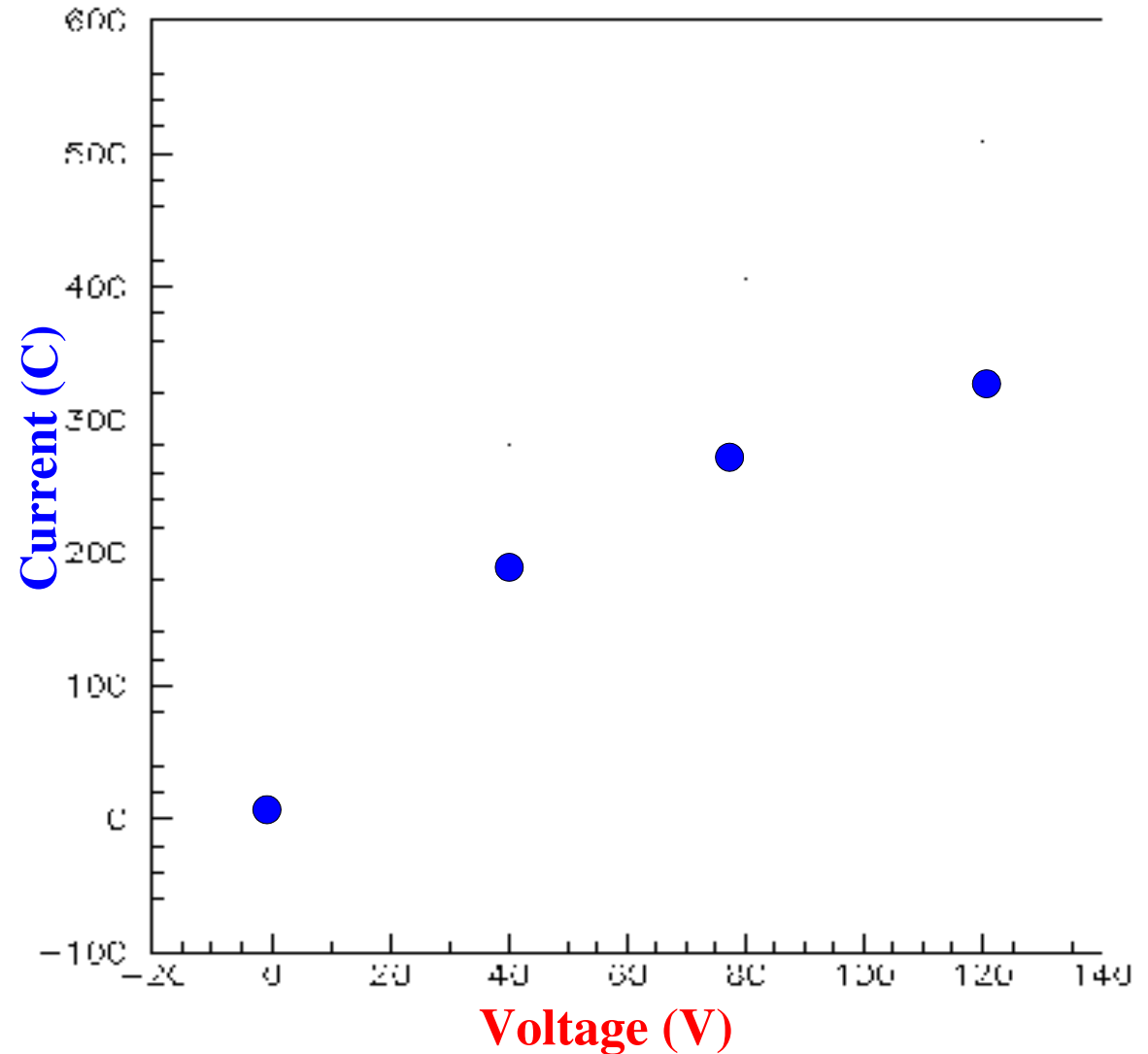

Electricity

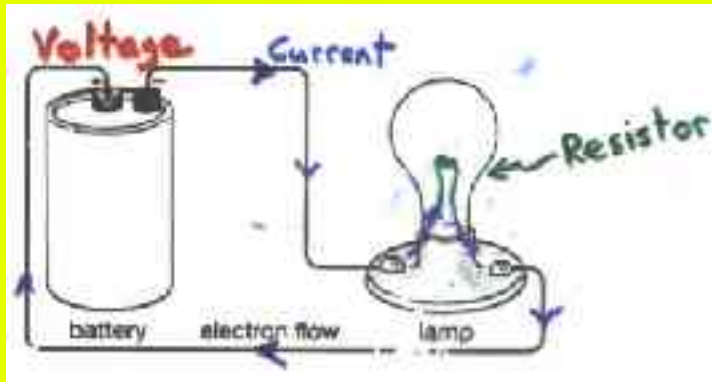
- Simple circuit to show how current depends on voltage:



Table


Voltage **Current**

0.	0.
40.	182.
80.	254.
120.	315.

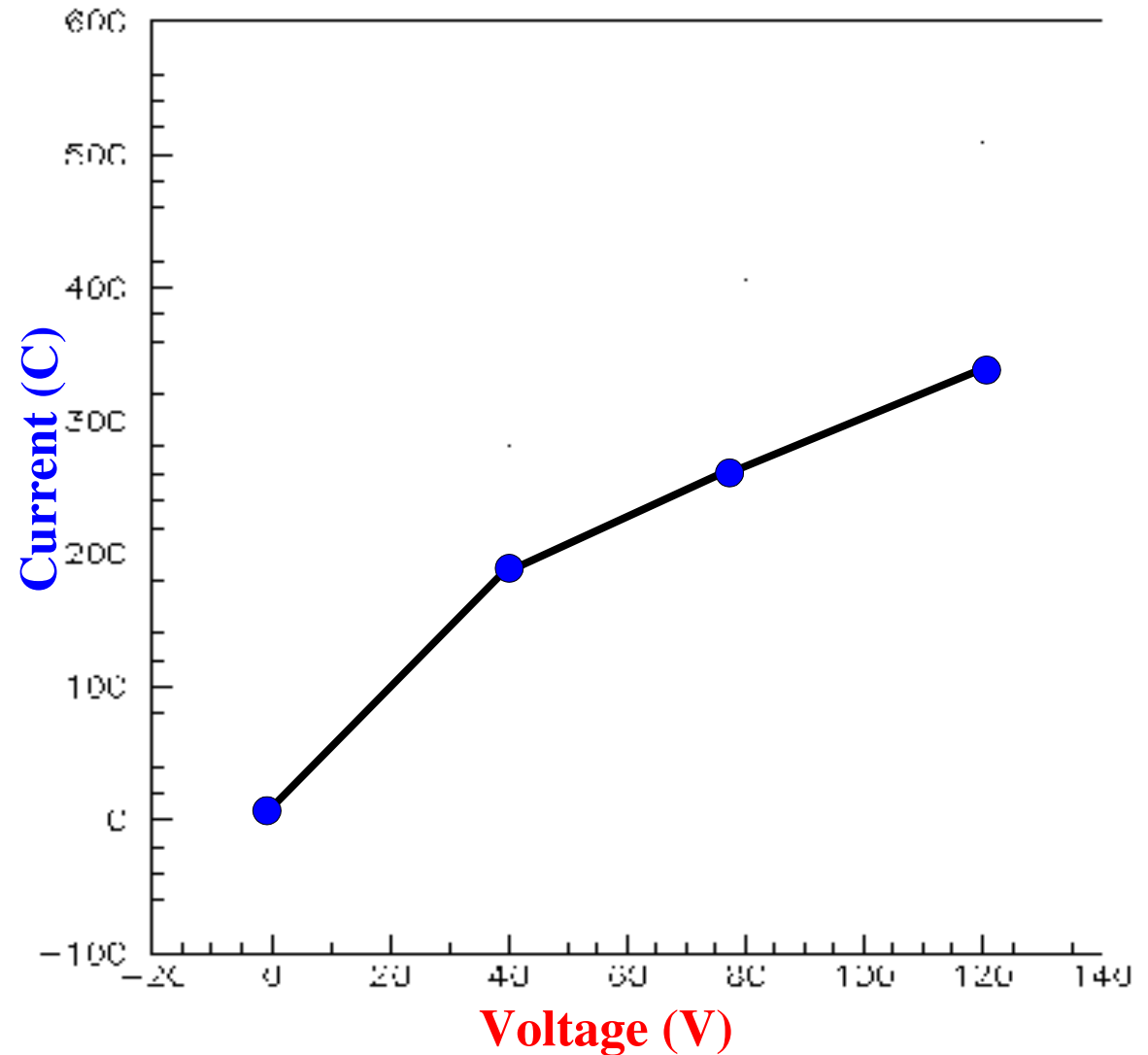

Electricity

- Series circuit of three light bulbs:

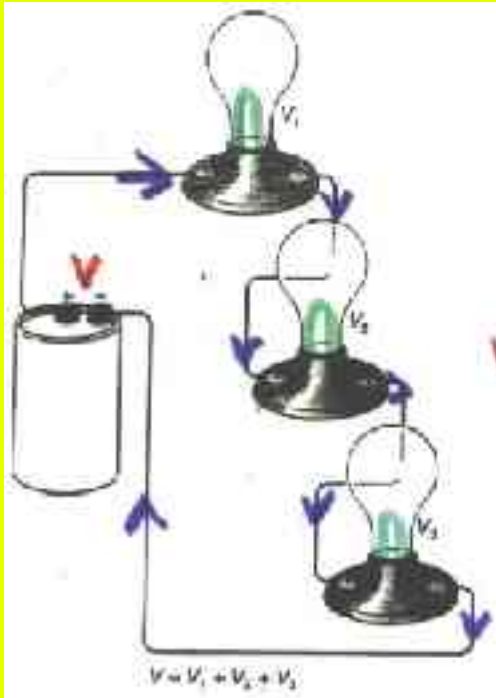

- Will bulbs be brighter or dimmer?
- What will happen if we remove one bulb?


Voltage – Pushes charges (current) through wires

Current – charges flowing through wire

Resistance tries to stop current!

Electricity

- Parallel circuit of three light bulbs:

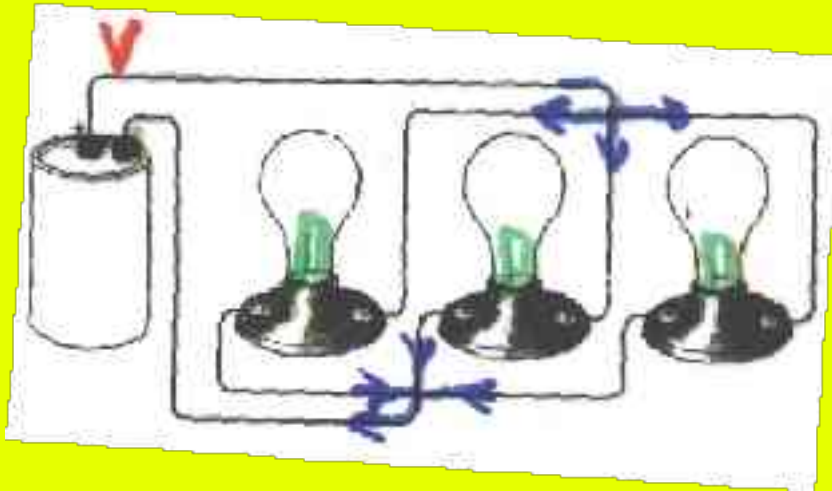

- Will bulbs be brighter or dimmer?
- What will happen if we remove one bulb?


Voltage – Pushes charges (current) through wires

Current – charges flowing through wire

Resistance tries to stop current!

Electricity

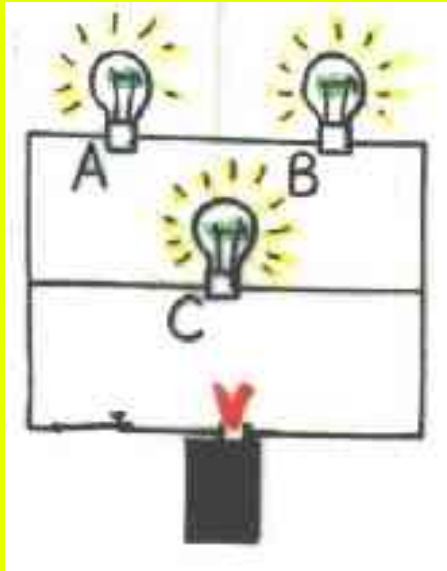- Combination circuit of three light bulbs:



- Which bulb will shine the brightest?
- What will happen if we remove bulb A?
- What will happen if we remove bulb C?



Voltage – Pushes charges (current) through wires

Current – charges flowing through wire

Resistance tries to stop current!

Electricity

- **Van De Graaff Generator**

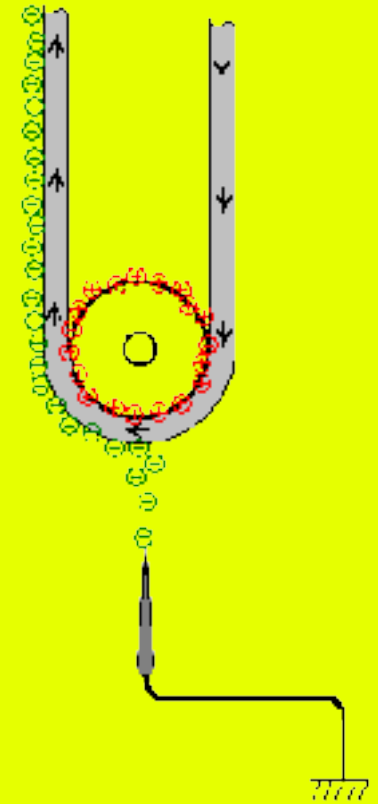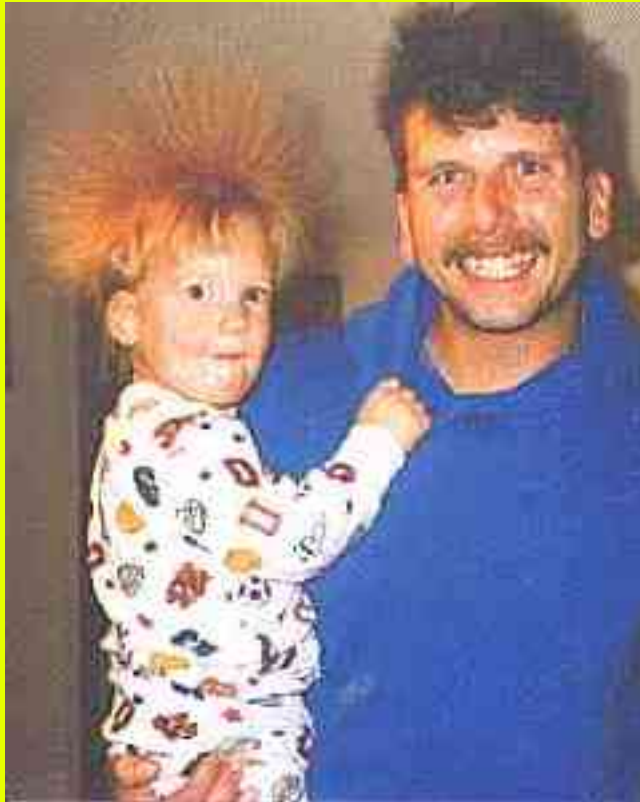


How charge is carried up to top


Electricity

- Capacitor Boom

Capacitor

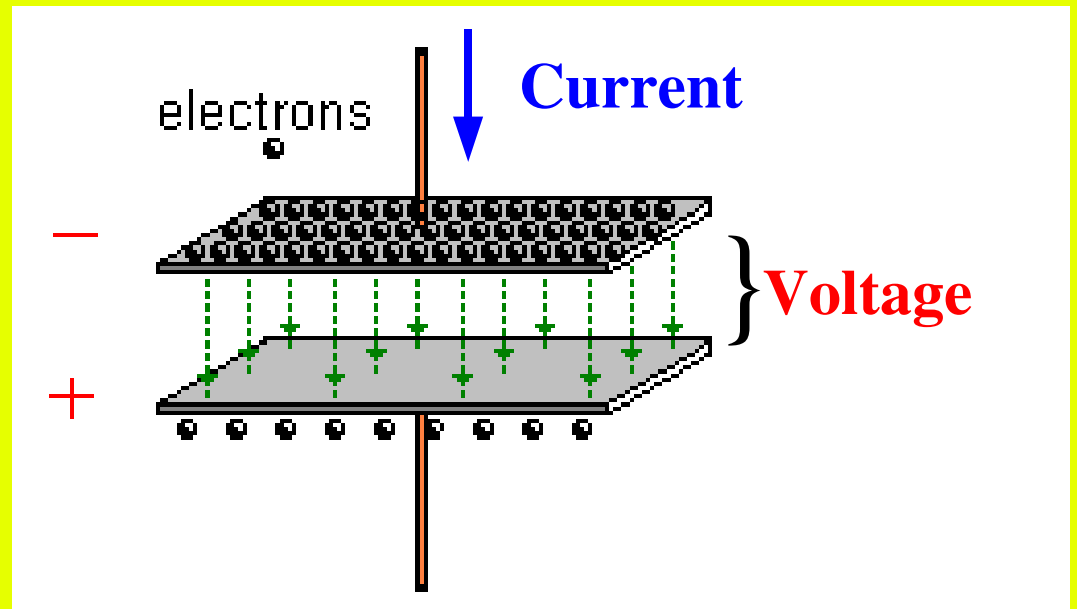


Circuit

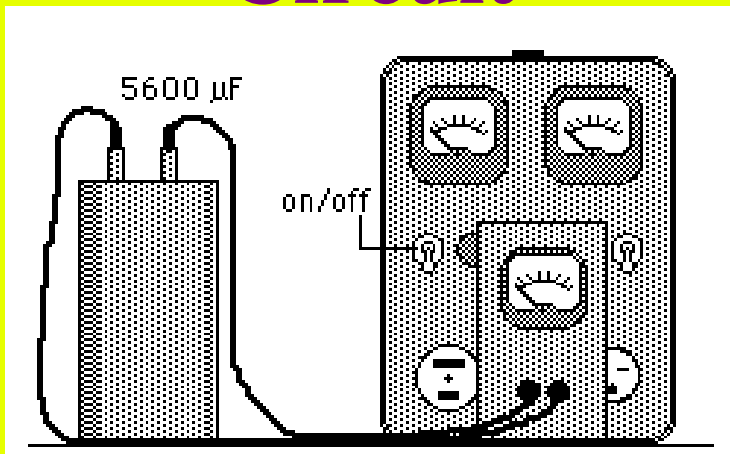

Electricity

- **LN2 Jumping Ring**

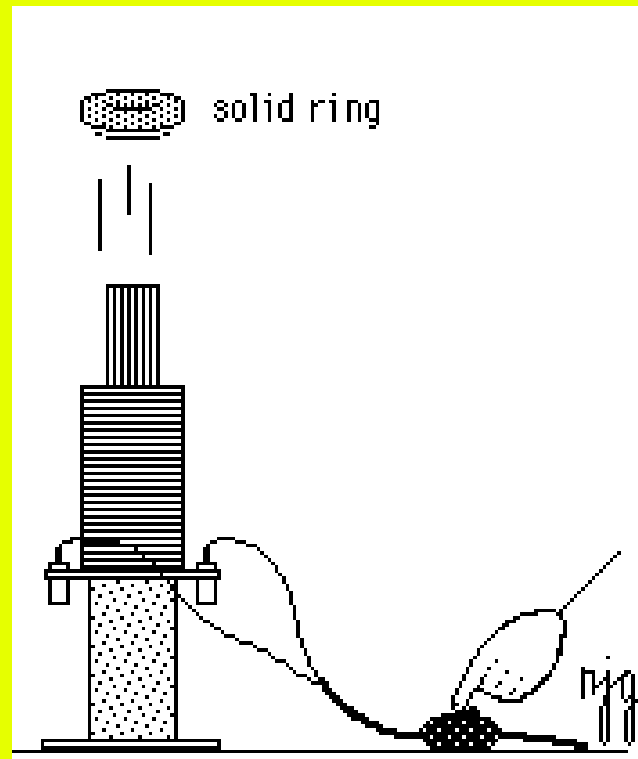


Electricity

- Summary:

- **Voltage (V)** depends on the distance between charges.



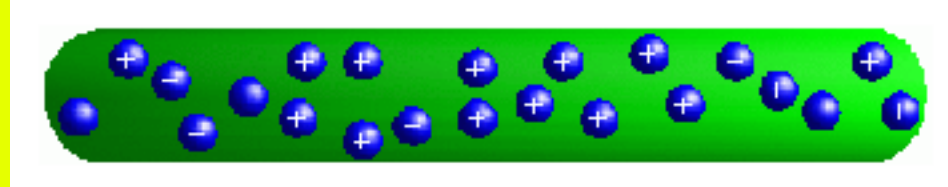- **Current (C)** depends on the number of moving charges.



- **Resistance (R)** depends on how much moving charges are slowed down

